

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## FINAL EXAMINATION

TRIMESTER 2, 2019/2020

**EMF4066 – RF CIRCUIT DESIGN**  
(TE)

9 MARCH 2020  
9:00 A.M. – 11:00 A.M.  
(2 Hours)


---

### INSTRUCTIONS TO STUDENTS


1. This Question paper consists of 9 pages with 4 Questions only.
2. Attempt **ALL FOUR** questions.
3. Please print all your answers in the Answer Booklet provided.

**Question 1**

- (a) A cascaded attenuator shown in Figure Q1(a) is used to reduce the source voltage to load  $R_L$ . It is required that the image impedance looking into the input of the attenuator be equal to the load resistor, such as  $Z_i = R_L$ .

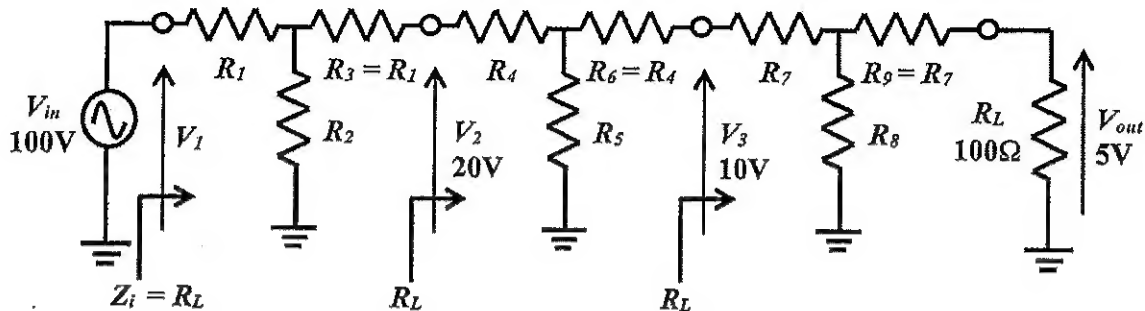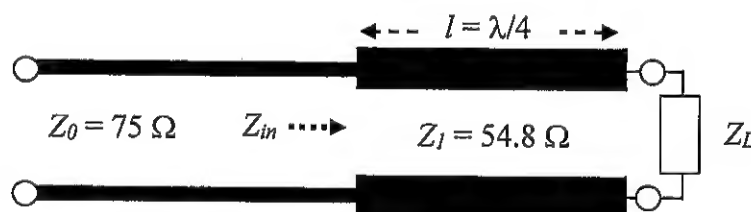**Figure Q1(a)**

- (i) State ONE (1) usage of attenuator in a typical RF application. [1 mark]
  - (ii) Name the type of attenuator used in the above circuit. [1 mark]
  - (iii) For each stage, determine the attenuation factor (in dB). What is the total attenuation factor (in dB) for this cascaded system? [4 marks]
  - (iv) Calculate the values of  $R_1, R_2, R_3, R_4, R_5, R_6, R_7, R_8$  and  $R_9$ . [9 marks]
- (b) Figure Q1(b) shows a quarter-wave matching transformer with characteristic impedance,  $Z_1 = 54.8 \Omega$  is used to match a load,  $Z_L$  to a  $75 \Omega$  lossless transmission line.

**Figure Q1(b)**

- (i) State TWO (2) advantages and TWO (2) disadvantages of using quarter-wave matching transformer in impedance matching, compared to conventional lumped element matching. [4 marks]

Continued .....

- (ii) Show that the characteristic impedance of the quarter-wave transformer

$$Z_1 = \sqrt{Z_0 \times Z_L}$$

where  $Z_0$  is the characteristic impedance of the lossless transmission line.

[4 marks]

- (iii) Determine  $Z_L$ .

[2 marks]

### **Question 2**

- (a) State FOUR (4) advantages and FOUR (4) disadvantages of microstrip lines in planar printed circuit board (PCB) implementations.

[8 marks]

- (b) Design a microstrip transmission line for a  $100\ \Omega$  characteristic impedance. The substrate thickness ( $d$ ) is 0.158 cm, with relative dielectric constant  $\epsilon_r = 2.2$ . What is the guide wavelength on this transmission line if the frequency is 4 GHz?

*(Hints – Use the microstrip equations listed in Appendix and assume  $W/d < 2$ )*

[8 marks]

- (c) A microwave transistor amplifier has the following  $S$ -parameters ( $Z_0 = 50\ \Omega$ ) measured at 5 GHz.

$$S_{11} = 0.641 \angle -171.3^\circ = -0.634 - j0.097,$$

$$S_{21} = 2.058 \angle 28.5^\circ = 1.809 + j0.982,$$

$$S_{12} = 0.057 \angle 16.3^\circ = 0.0547 + j0.0160 \quad \text{and}$$

$$S_{22} = 0.572 \angle -95.7^\circ = -0.0568 - j0.569.$$

- (i) Define the terms *unconditional stability* and *conditional stability* for a transistor amplifier.

[4 marks]


- (ii) Calculate the Rollette stability factor  $k$  and  $\Delta$ , and state the stability condition.

[5 marks]

**Continued .....**

**Question 3**

- (a) A filter has the  $S_{21}$  (in dB) shown in Figure Q3. It is measured from approximately 40 MHz to 1200 MHz, with a  $50\ \Omega$  reference impedance ( $Z_0$ ).

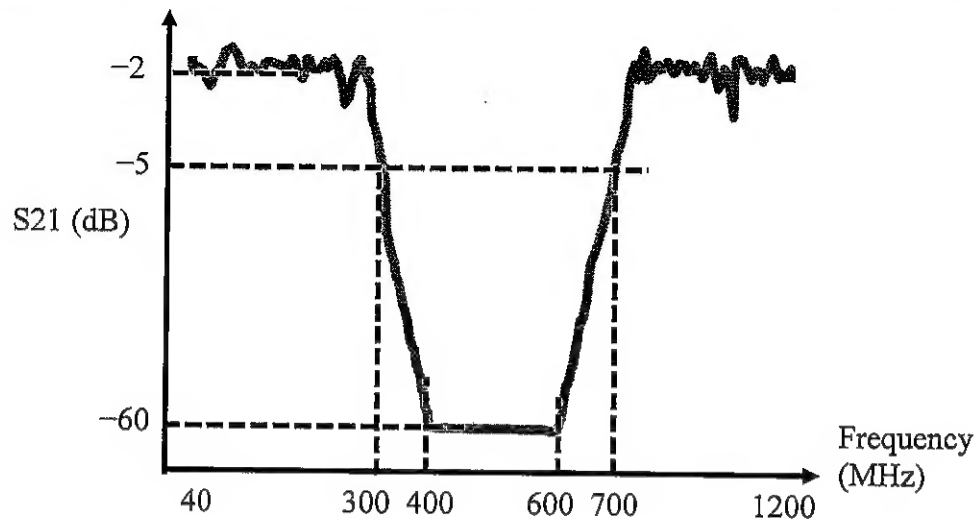**Figure Q3**

- (i) What type of filter is shown in the above measurement? [1 mark]
  - (ii) Determine the insertion loss, cut-off frequencies, center frequency and 3 dB bandwidth of the filter. [5 marks]
  - (iii) What are the pass-band frequencies, stop-band frequencies and rejections of the filter? [6 marks]
- (b) Design a stepped-impedance low-pass filter having a maximally flat (Butterworth) response and a cutoff frequency of 2.5 GHz. It is necessary to have more than 20 dB attenuation at 3.75 GHz. The filter impedance is  $50\ \Omega$ , the highest practical impedance is  $120\ \Omega$  and the lowest is  $20\ \Omega$ . Consider the filter is implemented with a microstrip FR-4 substrate (thickness,  $d = 0.158\text{ cm}$  and relative dielectric constant,  $\epsilon_r = 4.2$ ). Calculate all the required electrical lengths ( $\beta l_i$ ) along with the physical microstrip line widths ( $W_i$ ) and lengths ( $l_i$ ).

(Hints – Use the microstrip equations, Figure 1 and Table 2 in the Appendix)

[13 marks]

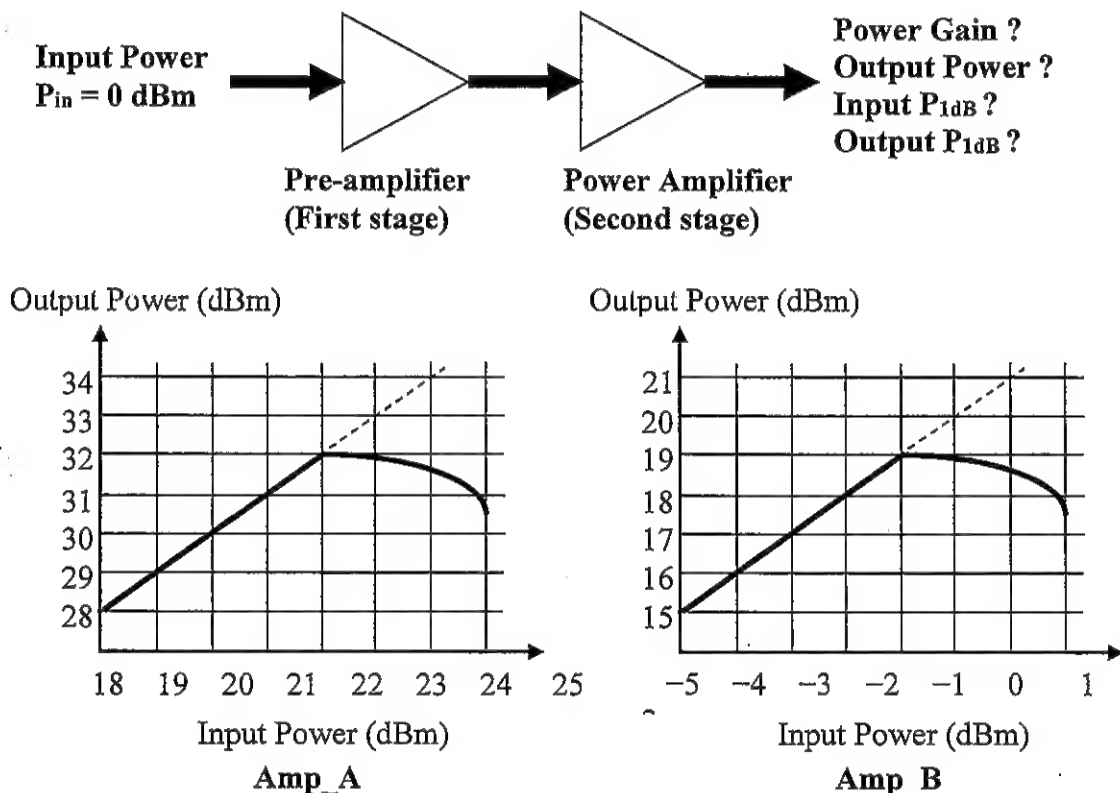
Continued .....

**Question 4**

- (a) Draw THREE (3) resistive negative feedback topologies each for both the Bipolar Junction Transistor (BJT) and Field Effect Transistor (FET) broadband amplifier.

[6 marks]

- (b) A two-stage power amplifier consisting of first stage pre-amplifier and second stage power amplifier for linear operation at 4 GHz, are to be designed. The input signal power is 0 dBm. The input and output power relationships for amplifiers **Amp\_A** and **Amp\_B** at 4 GHz, are shown in **Figure Q4(b)**. One will be used as pre-amplifier while the other will be the power amplifier.

**Figure Q4(b)**

- (i) Explain briefly the function and usage of pre-amplifier used in this design.
- (ii) Determine the linear power gain, 1 dB gain compression, input and output power at 1 dB gain compression for **Amp\_A**.

[4 marks]

Continued .....

- (iii) Determine the linear power gain, 1 dB gain compression, input and output power at 1 dB gain compression for **Amp\_B**.  
[4 marks]
- (iv) Which amplifier is suitable for the first stage? Explain your answer.  
[2 marks]
- (v) Which amplifier is suitable for the second stage? Explain your answer.  
[2 marks]
- (vi) Calculate the power gain and output power obtained after the first stage.  
[2 marks]
- (vii) Calculate the power gain and output power obtained from this design.  
[2 marks]

**Continued .....**

## Appendix – Useful Formulas

### Microstrip equations for dielectric constant and characteristic impedance

- The effective dielectric constant of a microstrip line is given by:

$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \cdot \frac{1}{\sqrt{1 + 12d/W}}$$

- Given the dimensions of microstrip line, characteristic impedance can be calculated as:

$$Z_0 = \begin{cases} \frac{60}{\sqrt{\epsilon_e}} \ln \left( \frac{8d}{W} + \frac{W}{4d} \right) & \text{for } W/d \leq 1 \\ \frac{120\pi}{\sqrt{\epsilon_e} \left[ \frac{W}{d} + 1.393 + 0.667 \ln \left( \frac{W}{d} + 1.444 \right) \right]} & \text{for } W/d \geq 1 \end{cases}$$

- For a given characteristic impedance and dielectric constant, the W/d ratio can be found as:

$$\frac{W}{d} = \begin{cases} \frac{8e^A}{e^{2A} - 2} & \text{for } W/d < 2 \\ \frac{2}{\pi} \left[ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right\} \right] & \text{for } W/d > 2 \end{cases}$$

where

$$A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left( 0.23 + \frac{0.11}{\epsilon_r} \right)$$

$$B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$

Continued .....

**Given:**

Input and Output reflection coefficient

$$\Gamma_1 = \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \quad \Gamma_2 = \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

Power Gain, Available Gain and Transducer Gain

$$G_P = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22}\Gamma_L|^2} \quad G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{(1 - |\Gamma_{out}|^2) |1 - S_{11}\Gamma_S|^2}$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - \Gamma_S\Gamma_{in})|^2 |1 - S_{22}\Gamma_L|^2}$$

Rollett factor

$$k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}||S_{21}|} \quad \text{and} \quad \Delta = S_{11}S_{22} - S_{12}S_{21}$$


Output and Input stability circles parameters center and radius

$$r_{out} = \frac{|S_{12}S_{21}|}{||S_{22}|^2 - |\Delta|^2|} \quad C_{out} = \frac{(S_{22} - S_{11}^*\Delta)^*}{|S_{22}|^2 - |\Delta|^2}$$

$$r_{in} = \frac{|S_{12}S_{21}|}{||S_{11}|^2 - |\Delta|^2|} \quad C_{in} = \frac{(S_{11} - S_{22}^*\Delta)^*}{|S_{11}|^2 - |\Delta|^2}$$

**Continued .....**

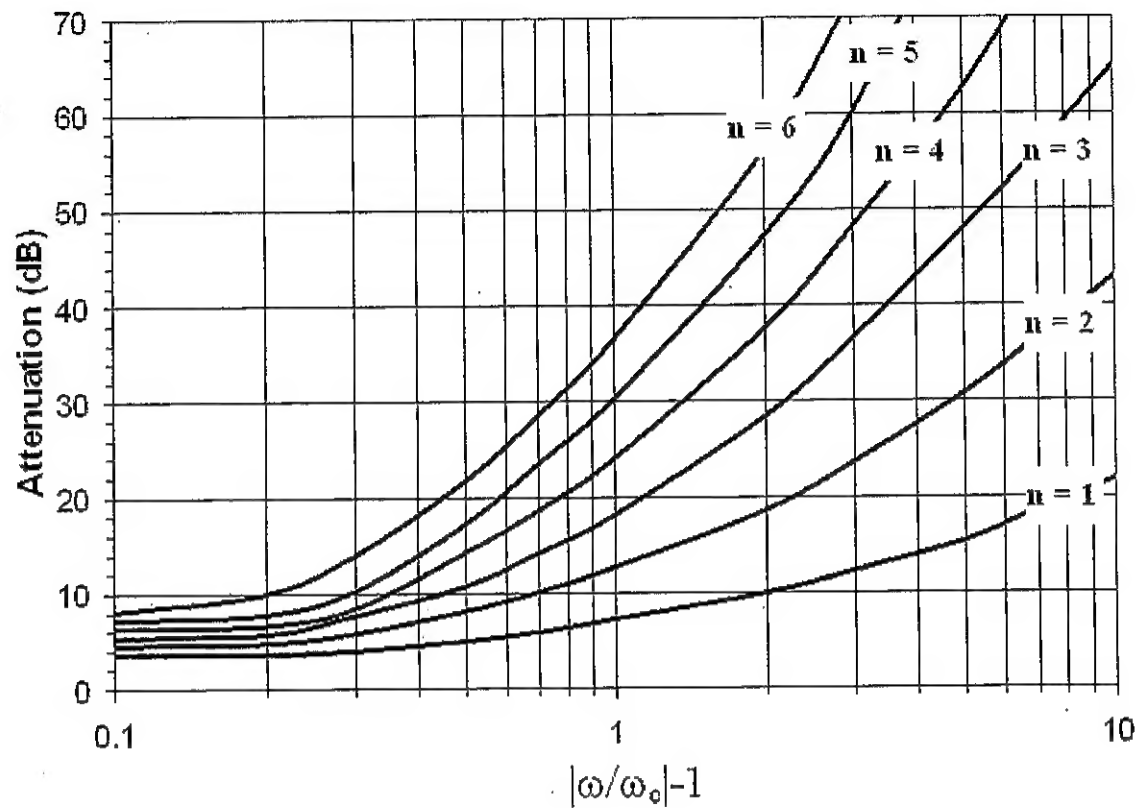

**Figure 1 – Attenuation versus normalized frequency for Butterworth prototypes****Table 2 – Element values for Butterworth Low-Pass Filter Prototype**

N	g1	g2	g3	g4	g5	g6	g7
1	2.000	1.000					
2	1.414	1.414	1.000				
3	1.000	2.000	1.000	1.000			
4	0.765	1.848	1.848	0.765	1.000		
5	0.618	1.618	2.000	1.618	0.618	1.000	
6	0.517	1.414	1.932	1.932	1.414	0.517	1.000

End of Page